

# Feedback current amplifier

Sanskar Nanegaonkar\*

The feedback current amplifier in Fig. 1.1 utilizes an op amp with an input differential resistance  $R_{id}$ , an open-loop gain  $\mu$ , and an output resistance  $r_o$ . The output current  $I_o$  that is delivered to the load resistance  $R_L$  is sensed by the feedback network composed of the two resistances  $R_M$  and  $R_F$  and a fraction  $I_f$ , is fed back to the amplifier input node.

Find expressions for  $G = \frac{I_o}{I_i}$ ,  $H = \frac{I_f}{I_o}$  and  $T = \frac{I_o}{I_s}$ , assuming that the feedback causes the voltage at the input node to be near ground. If the loop gain is large, what does the closed-loop current gain become? State precisely the condition under which this is obtained. For  $\mu = 10^4$ ,  $R_{id} = 1 \text{ M}\Omega$ ,  $r_o = 100 \text{ }\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  $R_M = 100 \text{ }\Omega$ , and  $R_F = 10 \text{ k}\Omega$ , find G, H, and T.

- Fig. 1.1 shows a feedback current amplifier. Draw the equivalent control system.

**Solution:** See fig 1.2

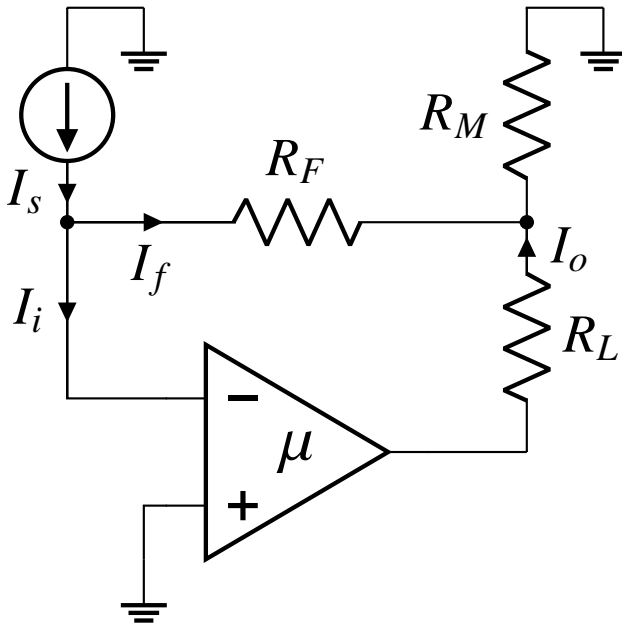


Fig. 1.1

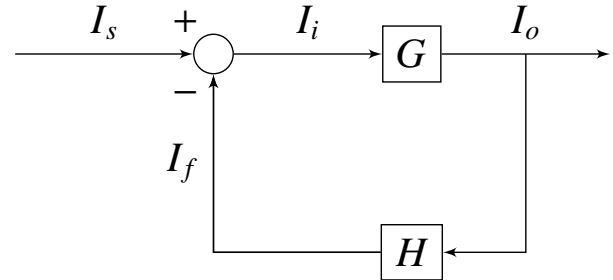


Fig. 1.2

- Refer table I for the parameters and draw the small signal equivalent model of the fig 1.1

**Solution:** See fig 2

Component	Description
$R_{id}$	Input Resistance of Op Amp
$R_{out}$	Output Resistance of Op Amp
$I_s$	Input Current
$I_o$	Output Current
$R_M, R_F$	Feedback Resistances
$R_L$	Load Resistance

TABLE I

- Given G (open-loop gain) as

$$G = \frac{I_o}{I_i} \quad (3.1)$$

Find G by considering the general open loop block diagram as shown in fig. 3 and fig. 2

**Solution:** Clearly from fig. 2, we can see that,

$$G = \frac{I_o}{I_i} = \mu \quad (3.2)$$

- Draw the block diagram and equivalent circuit for H (feedback factor).

**Solution:** Refer fig. 4.5 and 4.6

- Considering the feedback circuit as shown in fig. 4.6. Find  $R_{11}$  and  $R_{22}$ .

**Solution:** The value of  $R_{11}$  is obtained by

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

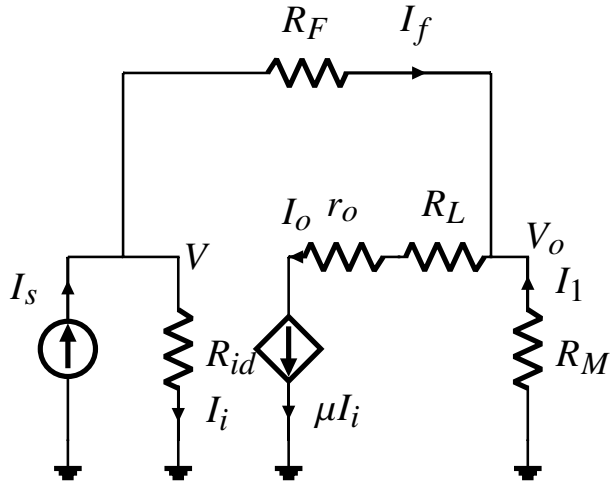


Fig. 2

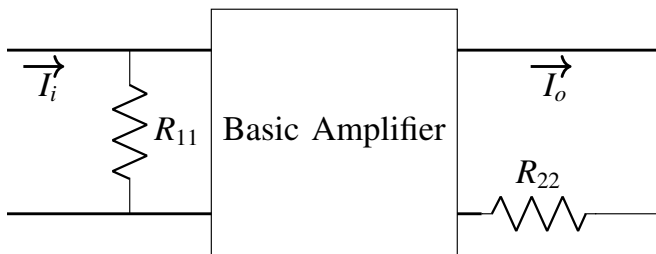


Fig. 3

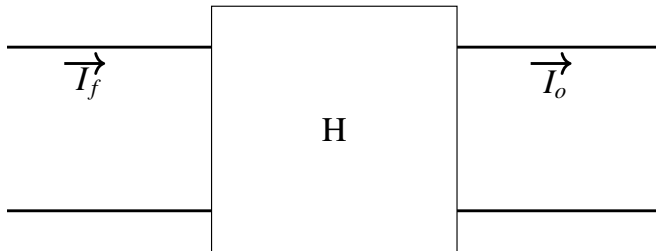


Fig. 4.5

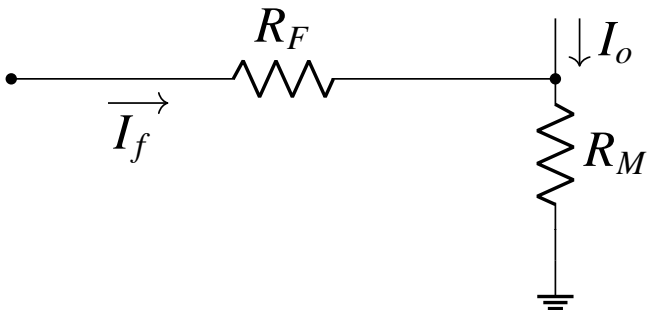


Fig. 4.6

open-circuited and the value of  $R_{22}$  is obtained by looking into port 2 (right) while it's port 1 is short-circuited.

$$R_{11} = R_F + R_M \quad (5.1)$$

$$R_{22} = R_F \parallel R_M \quad (5.2)$$

6. Given H as

$$H = \frac{I_f}{I_o} \quad (6.1)$$

Find H from fig. 4.6.

**Solution:** Using current division,

$$\frac{I_f}{I_o} = -\frac{R_M}{R_F + R_M} \quad (6.2)$$

$$\Rightarrow H = \frac{1}{1 + \frac{R_F}{R_M}} \quad (6.3)$$

7. Given T (closed-loop gain) as

$$T = \frac{I_o}{I_s} \quad (7.1)$$

Find T.

**Solution:** We know,

$$T = \frac{G}{1 + GH} \quad (7.2)$$

Therefore, from eq. 3.2 and 6.3, we get,

$$T = \frac{\mu}{1 + \frac{\mu}{1 + \frac{R_F}{R_M}}} \quad (7.3)$$

8. What will be closed-loop gain(T) if  $\mu \rightarrow \infty$

**Solution:** From eq. 7.3 we get,

$$T = \frac{\mu}{1 + \frac{\mu}{1 + \frac{R_F}{R_M}}} \quad (8.1)$$

$$T = \frac{1}{\frac{1}{\mu} + \frac{1}{1 + \frac{R_F}{R_M}}} \quad (8.2)$$

looking from port 1 (left) while it's port 2 is

Applying the limit, we get,

$$\Rightarrow T = 1 + \frac{R_F}{R_M} \quad (8.3)$$

9. Refer table II and find G, H and T

Component	Value
$\mu$	$10^4$
$R_{id}$	$1 \text{ M}\Omega$
$r_o$	$100 \text{ }\Omega$
$R_L$	$10 \text{ k}\Omega$
$R_M$	$100 \text{ }\Omega$
$R_F$	$10 \text{ k}\Omega$

TABLE II

**Solution:** Using eqs. 3.2, 6.3 and 7.3

We get,

$$G = \mu = 10^4 \quad (9.1)$$

$$H = \frac{1}{1 + \frac{R_F}{R_M}} = 9.9 \times 10^{-3} \quad (9.2)$$

$$T = \frac{\mu}{1 + \frac{\mu}{1 + \frac{R_F}{R_M}}} = 100 \quad (9.3)$$

10. Tabulate your results.

**Solution:** Refer table III,

Gain	Value
G	$10^4$
H	$9.9 \times 10^{-3}$
T	100

TABLE III

11. Simulate the circuit 1.1 using spice simulators and plot the generated output of the gains using python script

**Solution:** Refer fig. 11.7 and 11.8 for the plots.  
Find the netlist of the simulated circuit here:

```
codes/ep18btech11016/spice/
ep18btech11016.net
```

Python code used for generating the output:

```
codes/ep18betch11016/spice/
ep18btech11016.py
```

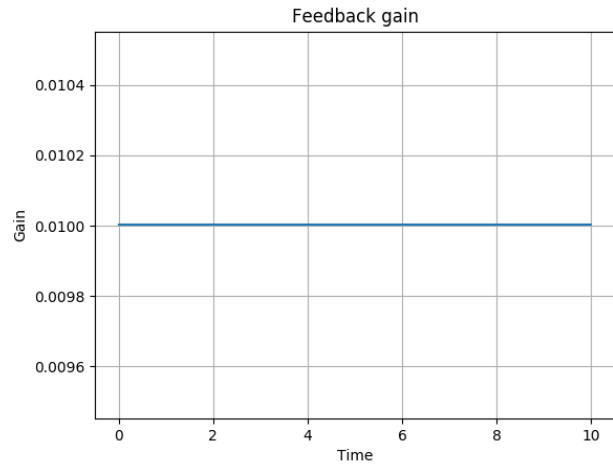


Fig. 11.7

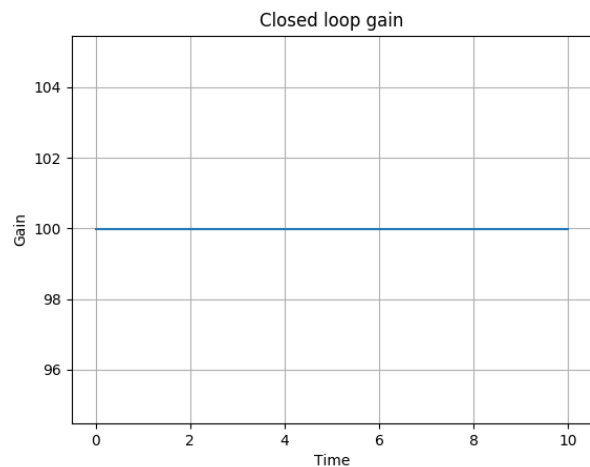


Fig. 11.8